

# Electricity & Circuits Provincial Exam Questions

Key

1. Which pair of values will cause the greatest deflection of an electron beam in a cathode ray tube?

	ACCELERATING VOLTAGE	DEFLECTION (PLATE) VOLTAGE
A.	400 V	20 V
B.	400 V	40 V
C.	800 V	20 V
D.	800 V	40 V


Do next unit

2. Electricity is transmitted at high potential to

- A. operate heavy equipment.
- B. maximize current in the transmission lines.
- C. minimize the energy lost as heat in the transmission lines.
- D. produce alternating currents because they always require high voltages.

next unit as well

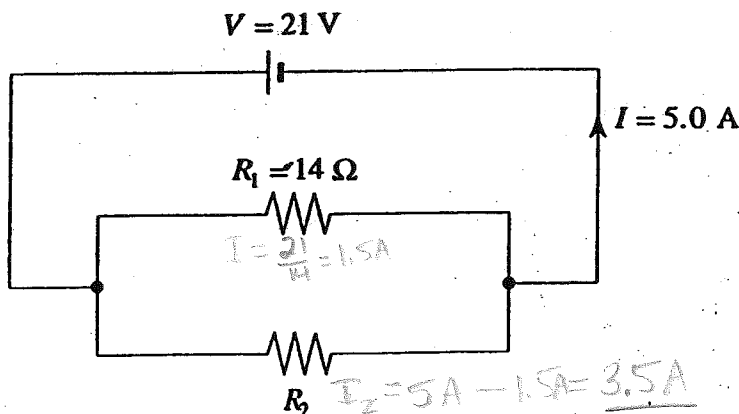3. Find the current flowing through resistor  $R_2$  in the circuit shown below.



4. A cell has an internal resistance of  $0.50 \Omega$ . It has a terminal voltage of  $1.4 \text{ V}$  when connected to a  $5.0 \Omega$  external resistance. What will its terminal voltage be if the  $5.0 \Omega$  resistor is replaced by a  $10.0 \Omega$  resistor?


$$V_t = \mathcal{E} - Ir \quad \text{①} \quad I = \frac{V_t}{R} = \frac{1.4 \text{ V}}{5 \Omega} = 0.28 \text{ A}$$

$$\text{②} \quad \mathcal{E} = V_t + Ir = 1.4 + 0.28(0.5) = 1.54 \text{ V} \quad \text{EMF is constant}$$

$$\text{③ add } R_{\text{new}} \quad I_{\text{new}} = \frac{\mathcal{E}}{R + r} = \frac{1.54 \text{ V}}{10.5 \Omega} = 0.146 \text{ A}$$

$$\text{④ then } V_t = \mathcal{E} - Ir = 1.54 - (0.146)(0.5) = 1.47 \text{ V}$$

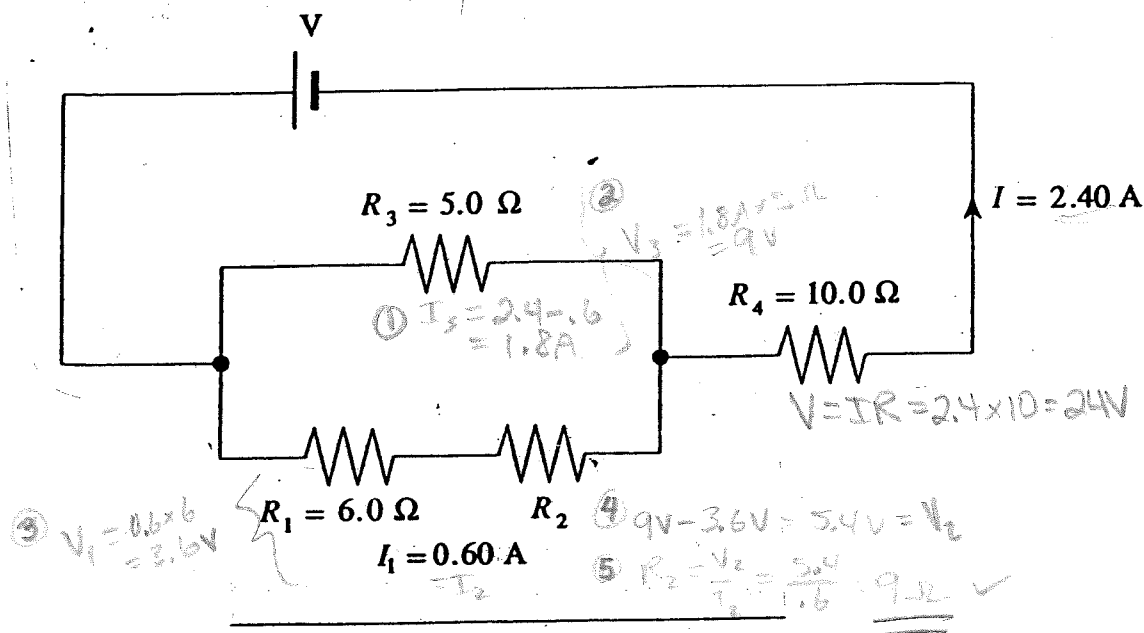5. a) Find the value of resistor  $R_2$ .



- b) Find the potential difference of the power supply  $V$ .


(2 marks)

$$24 \text{ V} + 9 \text{ V} = \underline{\underline{33 \text{ V}}}$$

6. Which household electrical appliance consumes the least energy in a typical month?

- A. Stove
- B. Dryer
- ☒ C. Clock
- D. Refrigerator

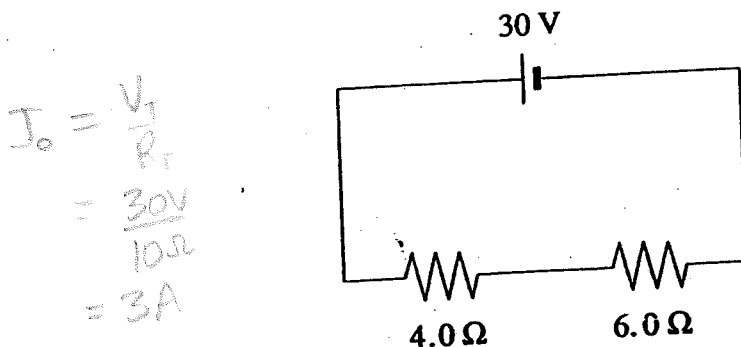7. What is the power output of the  $6.0 \Omega$  resistor in the diagram?



$$P = \frac{V^2}{R} = I^2 R$$

$$= (3)^2 (6 \Omega)$$


$$= \underline{\underline{54 \text{ W}}}$$

8. A  $12 \text{ V}$  power supply is connected to an  $8.0 \Omega$  resistor for  $50 \text{ s}$ . How much charge passes through the resistor?

$$I = \frac{V}{R} = \frac{12}{8} = 1.5 \text{ A}$$

$$Q = It = 1.5 \text{ A} \times 50 \text{ s} = \underline{\underline{75 \text{ C}}}$$

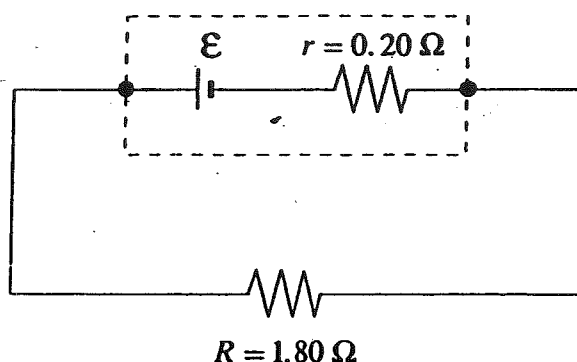9. The cell shown delivers a  $1.50 \text{ A}$  current to the external circuit and has a terminal voltage of  $2.70 \text{ V}$ .



- a) What is the emf of the cell?


$V_t = \mathcal{E} - Ir$   $\mathcal{E} = V_t + Ir = 2.70 \text{ V} + (1.50 \text{ A} \times 0.20 \Omega) = 3.0 \text{ V}$  (4 marks)

- b) The  $1.80 \Omega$  external resistance is replaced by other resistors and the current and terminal voltage are measured in each case. Using principles of physics, explain the relationship between terminal voltage  $V_t$  and current  $I$  as these resistors are changed?

$I = \frac{\mathcal{E}}{R_t}$  as  $R \uparrow$ ,  $I \downarrow$

$V_t = \mathcal{E} - Ir$  as  $I \downarrow$ ,  $V_t \uparrow$

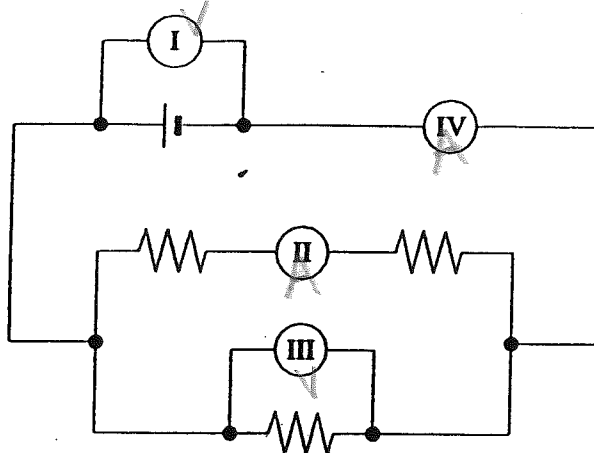
10. The circuit shown below includes two ammeters and two voltmeters. Identify the correct placement of these meters.




	AMMETERS	VOLTMETERS
A.	I, II	III, IV
B.	I, III	II, IV
C.	II, IV	I, III
D.	III, IV	I, II

11. A 120 V supply is connected to a heater of resistance  $15 \Omega$ . What must the resistance of another heater be in order to produce the same power output when connected to a 240 V supply?
- $P = \frac{V^2}{R} = \frac{120^2}{15} = 960 \text{ W}$ ;  $960 \text{ W} = \frac{(240)^2}{R} \rightarrow R = 60 \Omega$

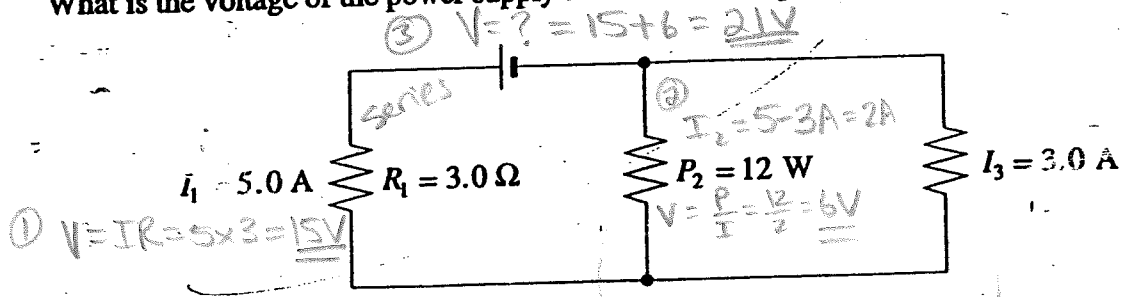12. What is the voltage of the power supply shown in the diagram?



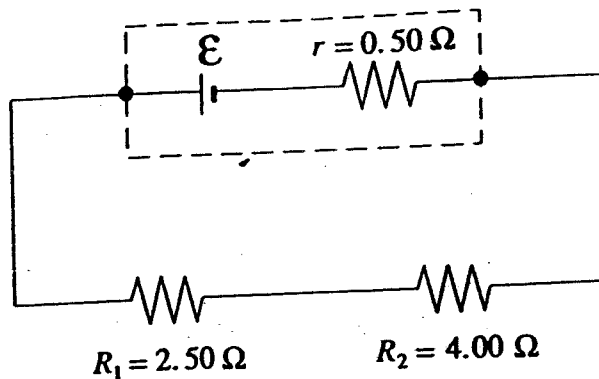13. The cell shown in the diagram supplies a 1.80 A current to the resistors  $R_1$  and  $R_2$ .



a)  $V_t = IR_t$   
 $= 1.8 \text{ A} \times (6.5 \Omega)$   
 $= 11.7 \text{ V}$


- a) What is the terminal voltage of the cell?

(3 marks)


- b) What is the emf of the cell?

$V_t = E - Ir$ ,  $E = V_t + Ir$  (4 marks)  
 $= 11.7 + (1.8)(0.5) = 12.6 \text{ V}$

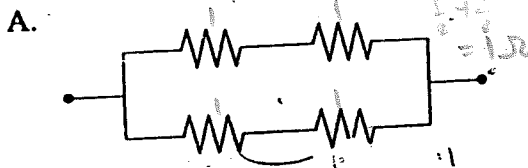
14. Which of the following arrangements would draw the largest current when connected to the same potential difference? All resistors have the same value. smallest R since  $I = \frac{V}{R}$




B.

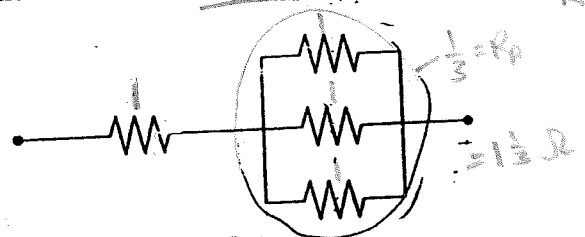

C.

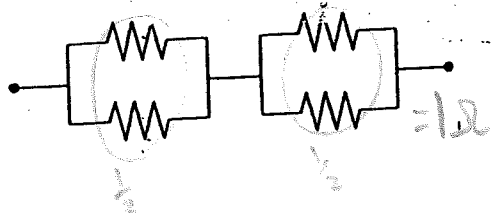


D.

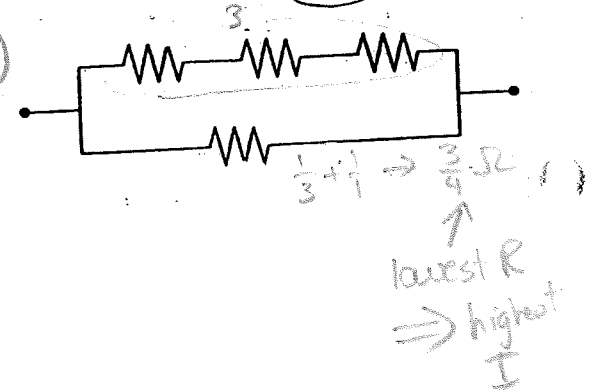


Find equivalent resistances

assume  $R = 1 \Omega$

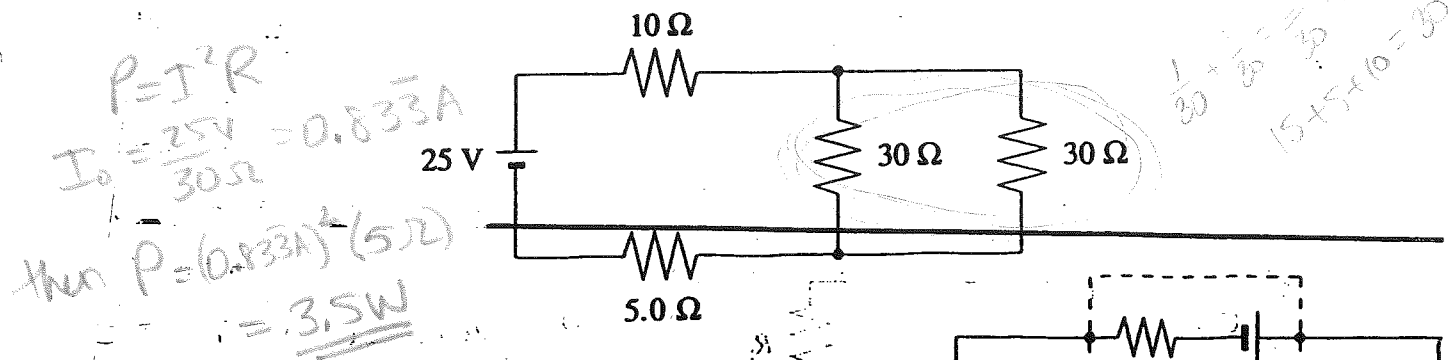
15. What is the power dissipated by the  $5.0\ \Omega$  resistor in the following circuit?



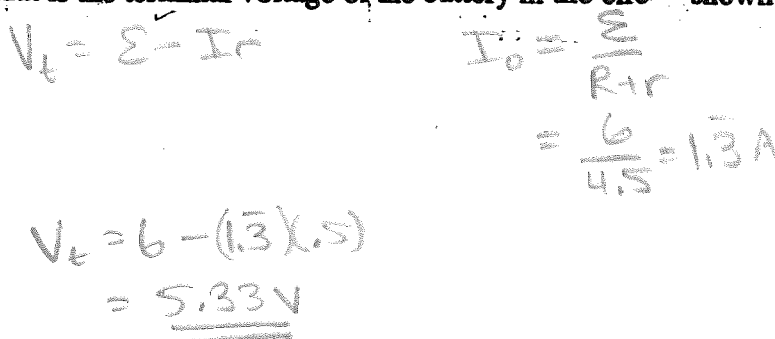16. What is the terminal voltage of the battery in the circuit shown



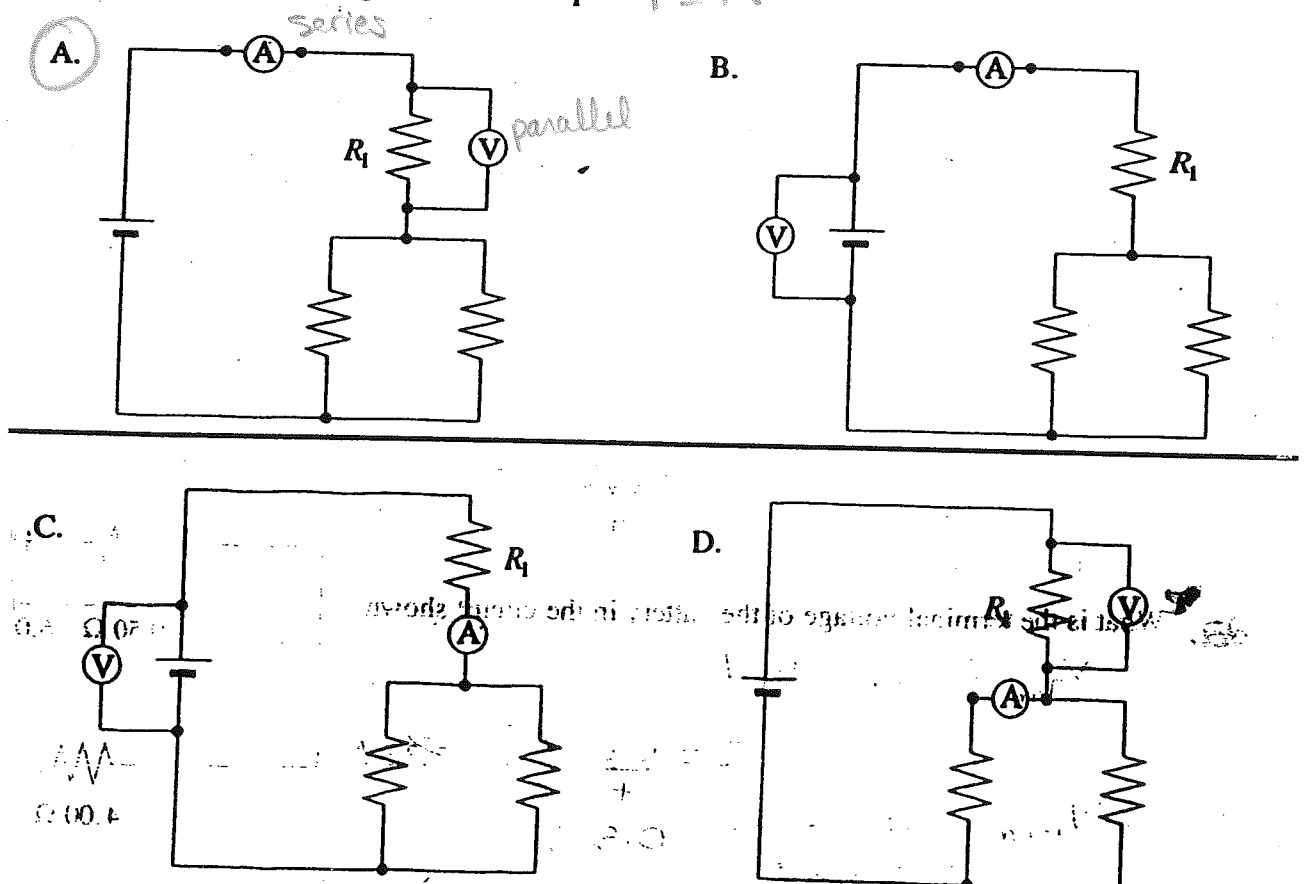
17. Which one of the following shows the correct placement of an ammeter and a voltmeter to determine the power output of resistor  $R_1$ ?  $P = IV$



18. The circuit shown consists of an 8.00 V battery and two light bulbs. Each light bulb dissipates 5.0 W. Assume that the light bulbs have a constant resistance. Switch S is open.

If a current of 1.50 A flows in the circuit, what is the internal resistance  $r$  of the battery?

(4 ma)

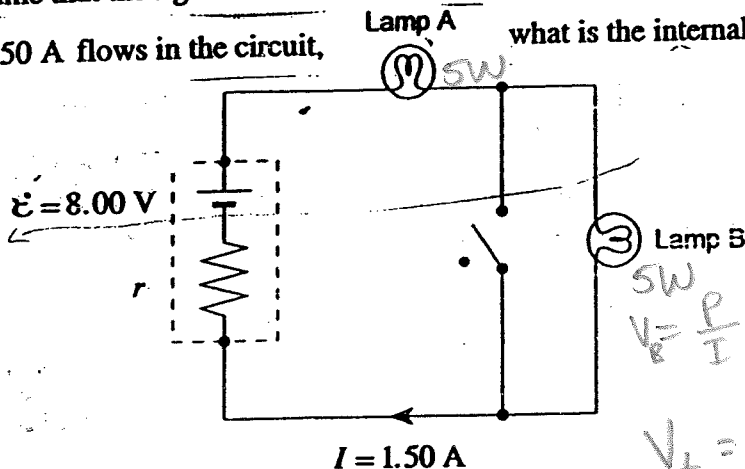

$$V_B = \frac{P}{I} = \frac{5W}{1.5A} = 3.33V = V_A$$


$$V_t = 2(3.33) = 6.66$$

$$V_t = \varepsilon - Ir$$


$$r = \frac{\varepsilon - V_t}{I} = \frac{8 - 6.66}{1.5} = 0.89 \Omega$$

19. In circuit one, resistors and voltmeters are connected as shown. In circuit two, an additional resistor  $R_4$  is placed in parallel with resistor  $R_2$ .

Circuit One

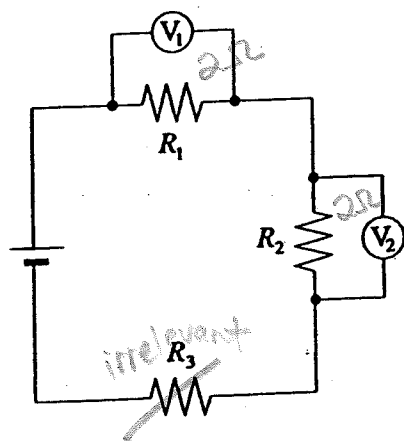

Circuit Two

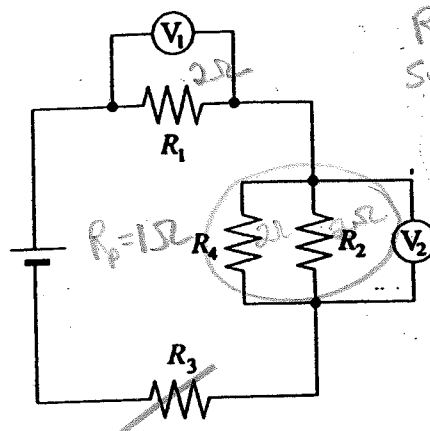


$V_2 = IR$   
 $R$  has  $\downarrow$   
 so  $V_2 \downarrow$   
 so  $V_1 \uparrow$   
 to use  
 voltage  
 not used  
 in  $V_2$

How have the values of  $V_1$  and  $V_2$  in circuit two changed compared to those in circuit one?

	$V_1$	$V_2$
A.	no change	decreased ✓
B.	decreased	increased
C.	increased ✓	decreased ✓
D.	increased ✓	no change

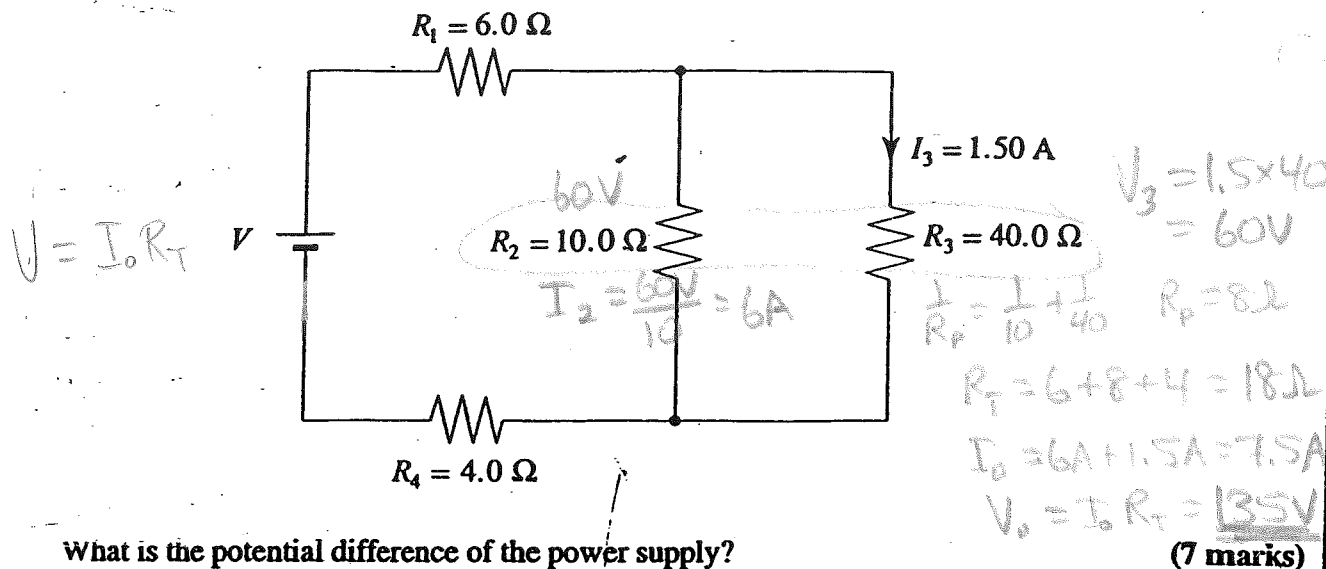
20. A current of 1.50 A flows through the 40.0  $\Omega$  resistor.




What is the potential difference of the power supply?

(7 marks)

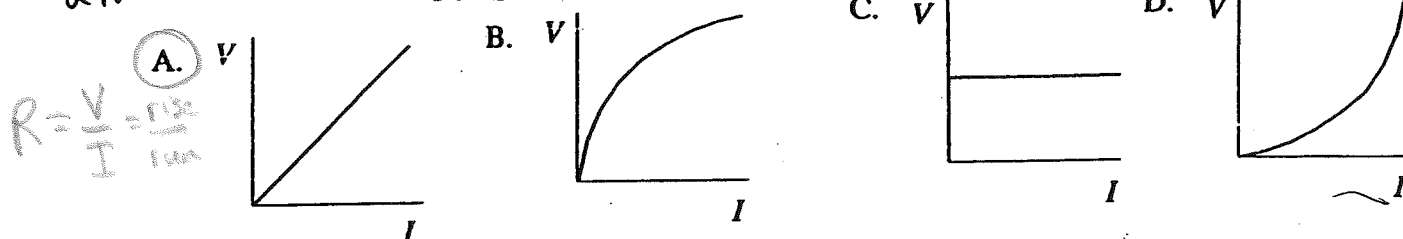
21. Which of the following graphs illustrates Ohm's law?



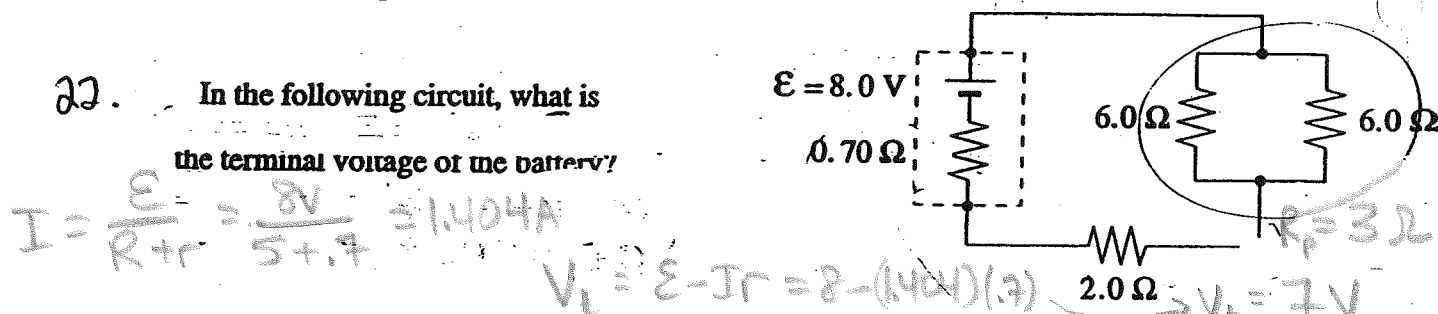22. In the following circuit, what is the terminal voltage of the battery?



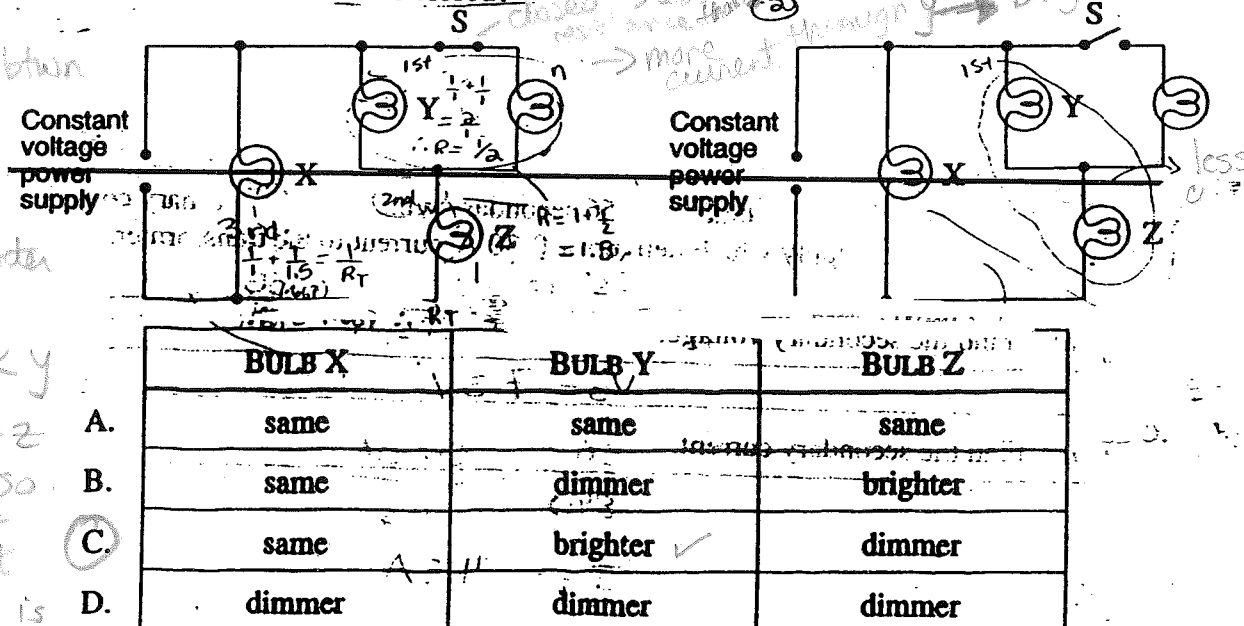
23. If switch S is opened, how does the brightness of each bulb (X, Y, and Z) compare to the situation when the switch was closed?



	BULB X	BULB Y	BULB Z
A.	same	same	same
B.	same	dimmer	brighter
C.	same	brighter	dimmer
D.	dimmer	dimmer	dimmer

24. What is the power dissipated in the  $8.0 \Omega$  resistor in the circuit as shown?


(7 marks)

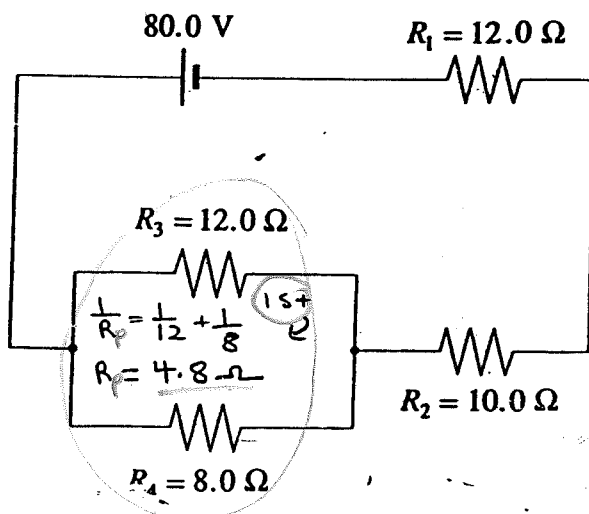


2nd  $R_T = 4.8 + 10 + 12$   
 $= 26.8 \Omega$   
 $I_0 = \frac{80V}{26.8 \Omega} = 2.985 A$   
 $I_4 = 2.985 A \times \frac{12 \Omega}{26.8 \Omega}$   
 $= 1.379 A$   
 $P = I^2 R = (1.379)^2 (8 \Omega)$   
 $= 25.7 W$

25. Which of the following combinations of three identical resistors has the least equivalent resistance?


A.

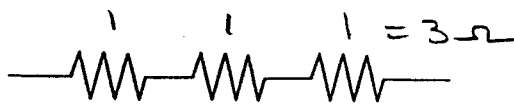


B.

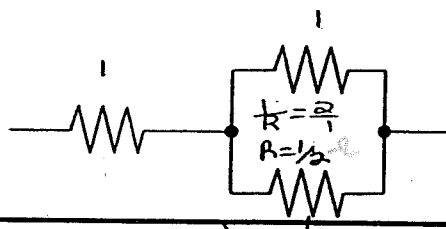

C.

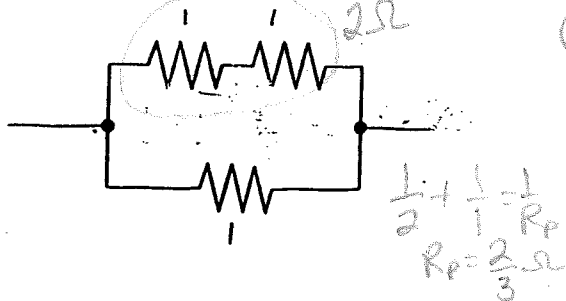

D.

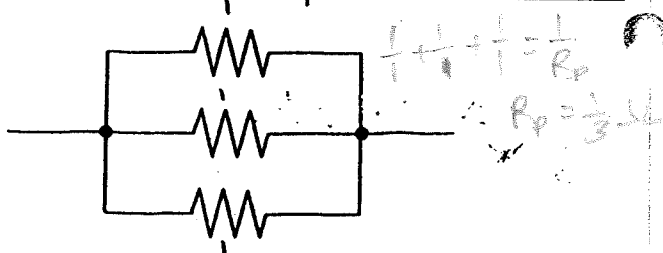


let each  $R = 1 \Omega$

26. An electrical device with a constant resistance draws  $0.75 A$  when connected to a  $4.8 V$  source. What are the current and power for this device when it is connected to a  $6.0 V$  source?

$R = \frac{V}{I} = \frac{4.8}{0.75} = 6.4 \Omega$   $I = \frac{V}{R} = \frac{6}{6.4} = 0.94 A$   $P = \frac{V^2}{R} = \frac{6^2}{6.4} = 5.6 W$

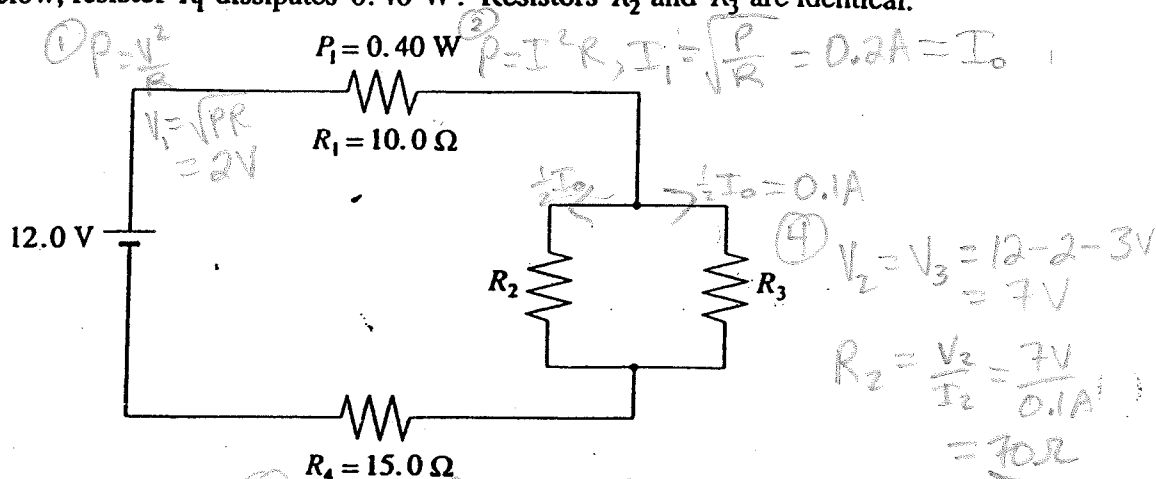27. In the circuit below, resistor  $R_1$  dissipates  $0.40 W$ . Resistors  $R_2$  and  $R_3$  are identical.



What is the resistance of  $R_2$ ?

③  $V_4 = I_0 R_4 = 0.2 \times 15 = 3V$

(7 marks)

- 8 -



# Electricity & Circuits Key

1. B
2. C
3. 3.5 A
4. 1.5 V
5. a)  $9\Omega$   
b) 33 V
6. C
7. 54 W
8. 75 C
9. a) 3 V  
b) as  $R \uparrow$ ,  $I \downarrow$  and  $V_t \uparrow$
10. C
11.  $60\Omega$
12. 21 V
13. a) 11.7 V  
b) 13 V
14. D
15. 3.5 W
16. 5.33 V
17. A
18.  $0.89\Omega$
19. C
20. 135 V
21. A
22. 7.0 V
23. C
24. 26 W
25. D
26. 0.94 A, 5.6 W
27.  $70\Omega$

